



BMS INSTITUTE OF TECHNOLOGY AND MANAGEMENT

Yelahanka, Bengaluru-64

DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION ENGINEERING

Course Name: Network Theory

Course Code: 18EC32

Sem: III ETE

Course Coordinator: Mr. Siddiq Iqbal

Date: 09/04/2022

Academic Year: 2021-22

CO5: conduct experiments and analyze on network theorems, prepare report for the same. **POs:** 5, 9,10,12
PSOs-1

“Modern Tool- Multisim”

Prepared by: S VARSHA (1BY20ET048)

Contents: Superposition Theorem

Thevenin's Theorem


Norton's Theorem

Superposition Theorem:

In any linear circuit, containing multiple independent, the current or voltage at any point in the network may be calculated as algebraic sum of the individual of each source acting alone.

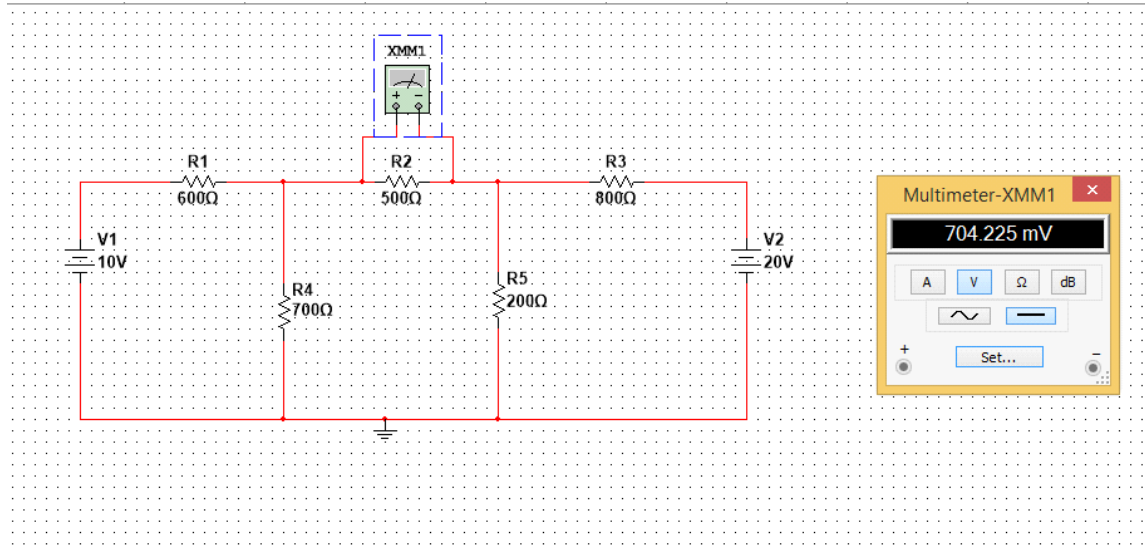
Problem:

Find the voltage across 500 ohm resistor in the given circuit using SPT.




Solution:

Consider 10V source

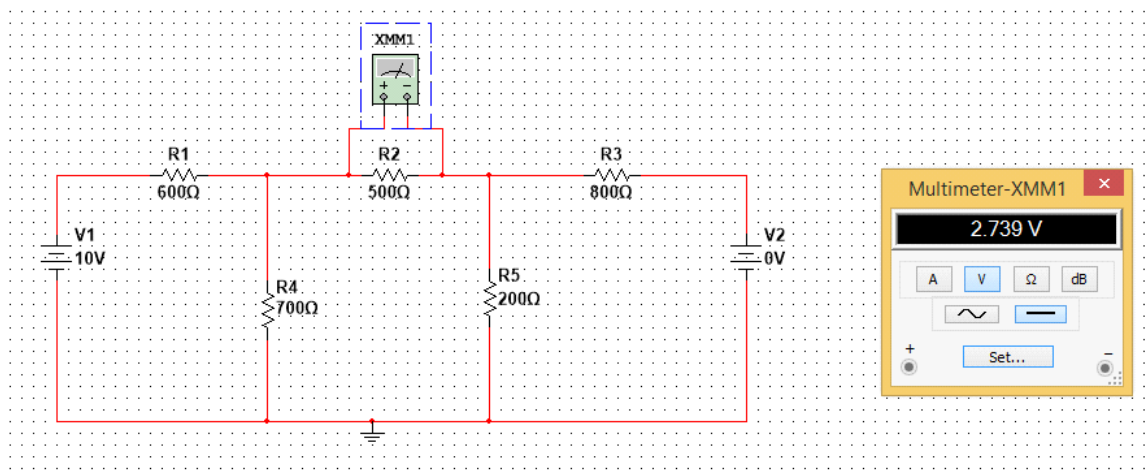

$$V_{R1} = 2.739 \text{ V}$$

Consider 20V source

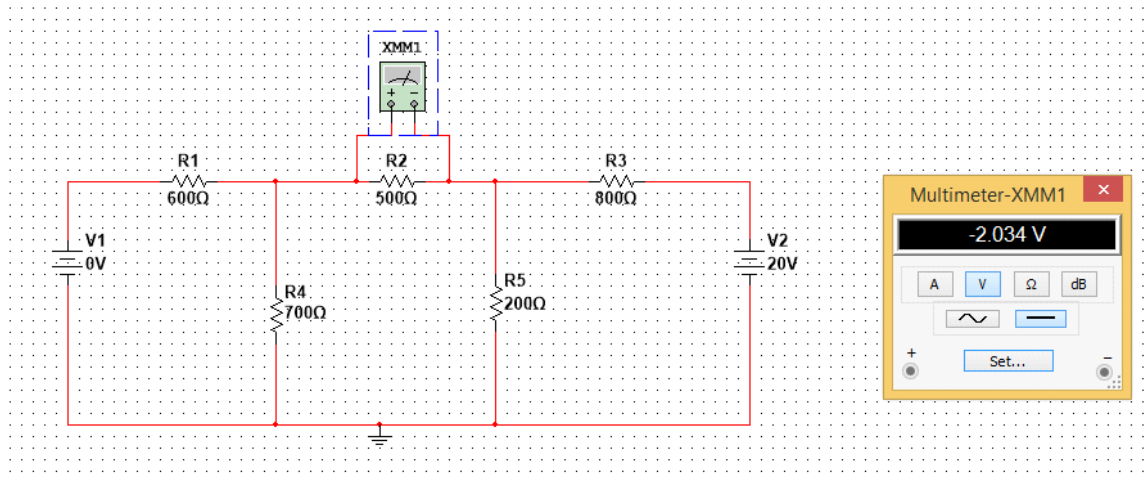

$$V_{R2} = -2.034 \text{ V}$$

By SPT we have,

$$V_{R1} + V_{R2} = V_R$$

$$2.739 + (-2.034) = 0.7 \text{ V}$$

$$V_R = 0.7 \text{ V}$$

The value that is obtained is same as the one that was found in circuit 1.

Thevenin's Theorem


It states that any two terminal linear network containing energy sources and impedances can be replaced with an equivalent circuit consisting of voltage source V_{th} in series with an impedance Z_{ph} .

V_{th} is the open circuit voltage between terminals of the network

Z_{ph} is the impedance measured between terminals of the network with all energy sources eliminated (but not their impedances).

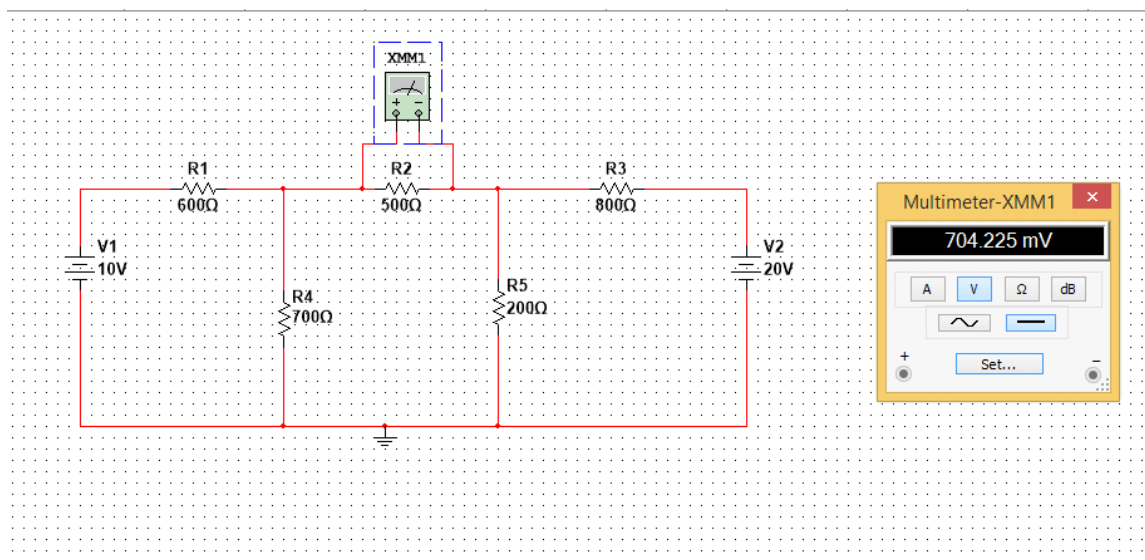
Problem:

Find the voltage across 500 ohm resistor using thevenin's theorem




Solution:

To find R_{th}

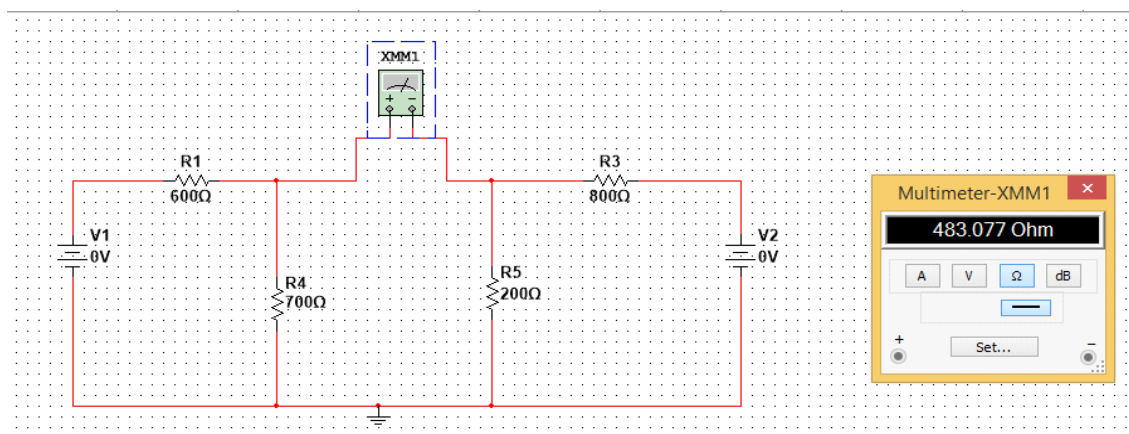


$$R_{th} = 483.077 \text{ ohm}$$

To find V_{oc}

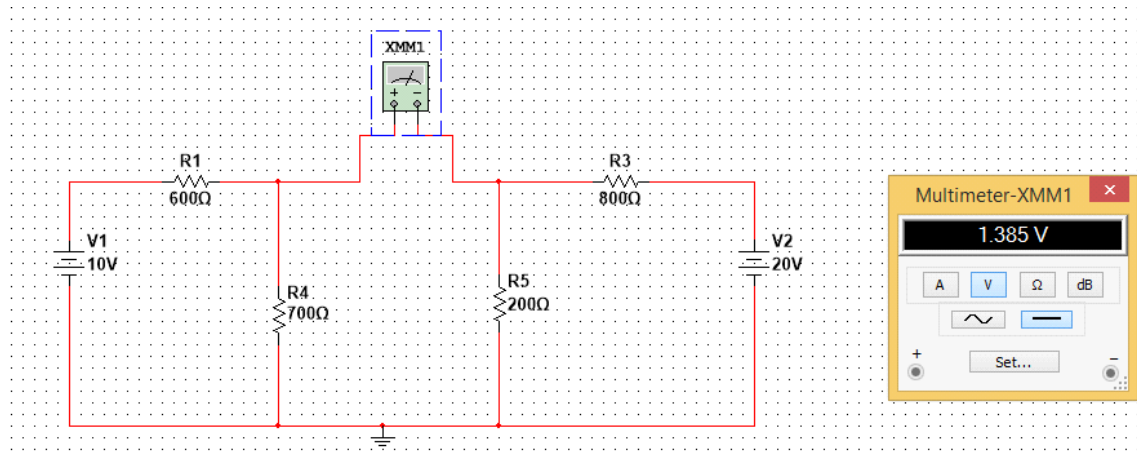

$$V_{oc} = 1.385 \text{ V}$$

Thevenin's equivalent:

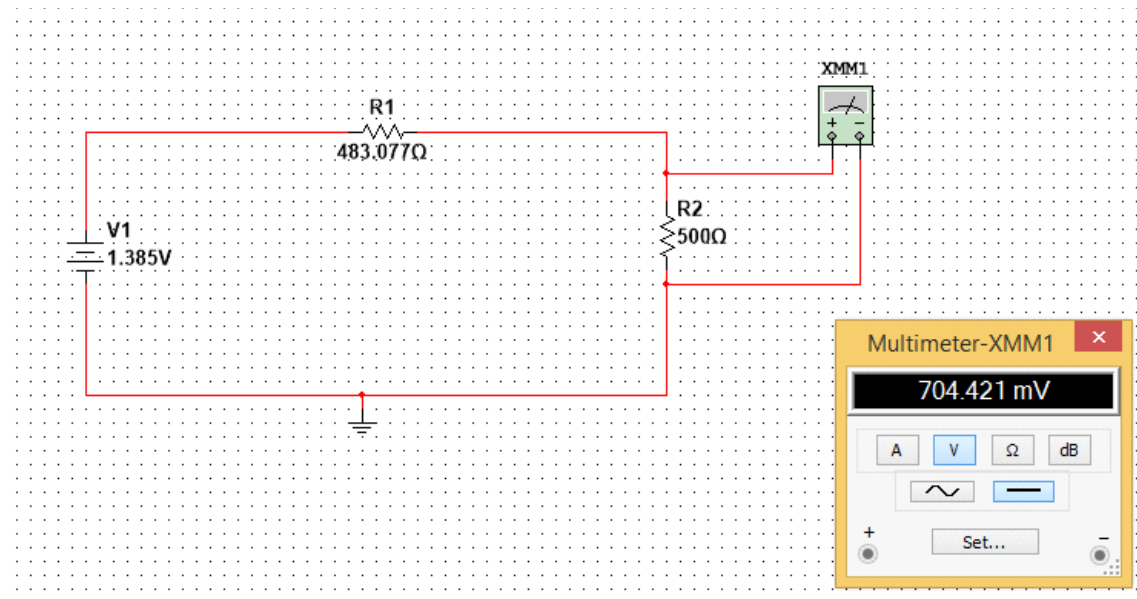

The voltage across 500 ohm is **0.7 V** by thevenin's theorem as obtained in circuit 1.

Norton's theorem

It states that a linear two terminal network can be replaced by an equivalent circuit consisting of a current source I_n in parallel with resistor R_n .

I_n is short circuit current to the terminals

R_n is the equivalent resistance when the independent sources are deactivated

Norton's theorem is the reciprocal of Thevenin's theorem.

Prepared by

S.Varsha

1BY20ET048

Acknowledgement :

It was a good experiment to perform. Thank you sir.